TINY MIPS CPU DESIGN

Joyce Berdkan
Electrical and Computer Engineering
George Washington University - GWU
District of Columbia, USA
j.berdkan@gwu.edu

Syed Hasan
Electrical and Computer Engineering
George Washington University - GWU
District of Columbia, USA
Syed.hasan@gwu.edu

***Abstract* - This paper presents the design, implementation, and verification of a multi-cycle Tiny MIPS CPU using Verilog HDL. The proposed processor follows a resource-efficient architecture in which a single datapath is reused across multiple cycles to execute instructions. The design integrates a finite-state control unit with a modular datapath comprising an ALU, register file, memory interface, and control logic. Functional verification is performed using self-checking testbenches and waveform analysis. The design is further evaluated through synthesis, scan insertion, and physical design stages, providing insights into timing, area, and power characteristics. The results demonstrate a correct and scalable CPU implementation suitable for educational and foundational processor design exploration.**

Index Terms – MIPS, Verilog HDL, CPU Design, Datapath, Control Unit, VLSI.

I. INTRODUCTION

Processor design is a fundamental aspect of digital system engineering, bridging theoretical computer architecture with practical hardware implementation. The MIPS architecture, known for its simplicity and modularity, serves as an ideal platform for understanding core processor design concepts.

This project implements a **multi-cycle Tiny MIPS CPU**, where instruction execution is divided into multiple stages such as fetch, decode, execute, memory access, and write-back. Unlike single-cycle architectures, the multi-cycle approach reuses hardware resources, reducing area and power consumption at the cost of increased execution cycles.

The system integrates a unified memory interface, instruction register (IR), memory data register (MDR), ALU, and control unit governed by a finite-state machine (FSM). The design flow includes RTL modeling, functional verification, synthesis, design-for-test (DFT), and physical layout generation, providing a complete ASIC design experience.

II. SYSTEM OVERVIEW (SYSTOLIC EXECUTION MODEL)

A. Datapath Overview

The datapath consists of interconnected hardware modules responsible for executing instructions. As illustrated in the datapath diagram, key components include:

- Program Counter (PC) and PCNext logic
- Instruction Register (IR)
- Register File (8 registers: $s0–$s7)
- Arithmetic Logic Unit (ALU)
- ALUOut register for intermediate storage
- Memory interface (shared instruction/data memory)
- Multiplexers for operand selection

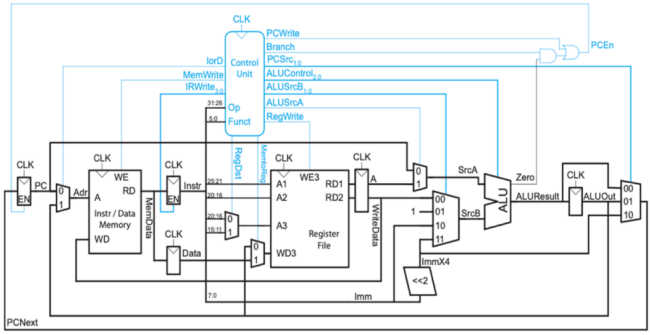

Figure 1: Data Path Diagram

B. Control Unit

The control unit generates signals such as:

- PCWrite, MemWrite, RegWrite
- ALUSrcA, ALUSrcB
- MemtoReg, RegDst
- PCSrc

These signals coordinate datapath operations across multiple clock cycles.

C. Instruction Set

The CPU supports a subset of MIPS instructions including:

- **R-type:** add, sub, and, or, slt
- **I-type:** addi, lb, sb
- **Control flow:** beq, j

The **instruction encoding table** defines opcode and function fields.

Instruction	Function		Encoding	op	funct
`add $1, $2, $3`	addition:	$1 ← $2 + $3	R	000000	100000
`sub $1, $2, $3`	subtraction:	$1 ← $2 – $3	R	000000	100010
`and $1, $2, $3`	bitwise and:	$1 ← $2 and $3	R	000000	100100
`or $1, $2, $3`	bitwise or:	$1 ← $2 or $3	R	000000	100101
`slt $1, $2, $3`	set less than:	$1 ← 1 if $2 < $3 $1 ← 0 otherwise	R	000000	101010
`addi $1, $2,`	add immediate:	$1← $2 + imm	I	001000	n/a
`beq $1, $2, imm`	branch if equal:	PC ← PC + imm[a]	I	000100	n/a
`j destination`	jump:	PC_destination[a]	J	000010	n/a
`lb $1, imm($2)`	load byte:	$1 ← mem[$2 + imm]	I	100000	n/a
`sb $1, imm($2)`	store byte:	mem[$2 + imm] ← $1	I	110000	n/a

Figure 2: Instruction Encoding Table

III. CONTROL DESIGN (FSM)

The processor operation is governed by a **finite-state machine**, which sequences instruction execution.

The **FSM diagram** shows states such as:

1. Instruction Fetch
2. Instruction Decode
3. Execution
4. Memory Access
5. Write-back

Each state activates specific control signals to drive datapath components. For example:

- Fetch → PC update + memory read
- Decode → register access
- Execute → ALU operation
- Memory → load/store
- Write-back → register update

This structured sequencing ensures correct multi-cycle execution.

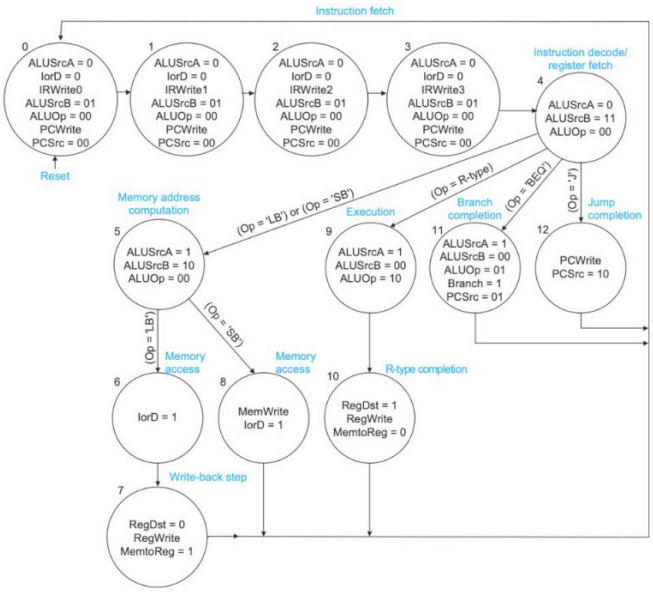

Figure 3 : FSM Diagram

IV. RTL IMPLEMENTATION

The Tiny MIPS CPU was implemented in Verilog HDL using a modular RTL design approach. The complete processor is divided into a top-level integration module, a finite-state controller, a datapath, ALU control logic, and supporting sequential and combinational blocks.

A. Top-Level CPU Module: mips.v

The mips.v module is the top-level processor wrapper. It connects the controller, ALU control unit, and datapath. The external interface includes the clock, reset, memory data input, memory read/write control signals, memory address, and write-data output.

The controller receives the opcode field from the instruction and the zero flag from the datapath. It then generates control signals such as memread, memwrite, alusrca, memtoreg, iord, pcen, regwrite, regdst, pcsource, alusrcb, aluop, and irwrite. The ALU control module converts aluop and the instruction function field into the final ALU operation code.

B. Controller Module: controller.v

The controller is designed as a finite-state machine that sequences the multi-cycle execution of each instruction. It contains states for instruction fetch, decode, memory address calculation, memory read, memory write, R-type execution, R-type write-back, branch completion, jump completion, addi execution, and addi write-back.

The instruction fetch process is divided into four states because the memory interface is 8 bits wide while the instruction word is 32 bits. Each fetch state loads one byte of

the instruction into the instruction register using the 4-bit irwrite signal.

The controller supports the following opcodes:

Instruction Type	Opcode
R-type	**000000**
addi	**001000**
beq	**000100**
jump	**000010**
lb	**100000**
sb	**101000**

Figure 4: Table represents instruction Type and Opcode.

C. Datapath Module: datapath.v

The datapath module implements the main execution hardware of the CPU. It contains the program counter, instruction register, memory data register, register file, ALU, ALUOut register, multiplexers, and zero detection logic.

D. ALU Module: alu.v

The ALU performs the arithmetic and logical operations required by the supported Tiny MIPS instruction set. It accepts two 8-bit operands and a 3-bit ALU control input.

ALU Control	Operation
000	AND
001	OR
010	ADD
110	SUB
111	SLT

Figure 5: Table represents ALU Control and Operation.

The SLT operation uses signed comparison and produces 8'd1 when operand a is less than operand b; otherwise, it produces 8'd0.

E. ALU Control Module: alucontrol.v

The ALU control block translates the high-level aluop signal from the controller and the instruction funct field into the 3-bit ALU operation code.

For load, store, addi, fetch, and address calculation, aluop = 00 selects addition. For branch-equal, aluop = 01 selects subtraction. For R-type instructions, aluop = 10 enables decoding of the function field.

F. Register File Module: regfile.v

The register file contains eight 8-bit registers corresponding to the simplified register set $s0 through $s7. It supports two asynchronous read ports and one synchronous write port.

G. Sequential Storage Modules

Three sequential modules are used throughout the datapath:

Module	Function
flop.v	8-bit positive-edge D flip-flop
flopen.v	8-bit flip-flop with enable
flopenr.v	8-bit flip-flop with enable and reset

Figure 6: Table Represents Sequential Storage Modules and its functions

The program counter uses flopenr so that it can be reset to address 0x00 and updated only when pcen is asserted.

H. Multiplexer Modules

The design uses three multiplexer modules:

Module	Width	Purpose
mux2.v	8-bit	Selects between two datapath inputs
mux4.v	8-bit	Selects among four datapath inputs
mux23.v	3-bit	Selects register destination address

Figure 7: Table Represents Multiplexer Modules, width and its purpose

These multiplexers allow the same ALU and datapath hardware to be reused across different instruction types.

I. Zero Detection Module: zerodetect.v

The zero-detection module checks whether the ALU result is equal to zero. Its output is used by the controller during beq execution. If the subtraction result is zero, the branch condition is true and the PC is updated.

J. Memory Module: ram.v

The ram.v module models a 256-word, 8-bit memory used for instruction and data storage during simulation. It is initialized using ram.dat. The memory performs reads and writes on the negative clock edge, which separates memory access timing from positive edge datapath register updates.

K. RTL Hierarchy Summary

mips.v
- *controller.v*
- *alucontrol.v*
- *datapath.v*
  - *regfile.v*
  - *alu.v*
  - *zerodetect.v*
  - *flop.v*
  - *flopen.v*
  - *flopenr.v*
  - *mux2.v*

```
├── mux4.v
└── mux23.v
```

Figure 7: Figure Represents RTL Hierarchy

This modular RTL structure improves readability, simplifies debugging, and allows each block to be individually verified before complete CPU-level simulation.

V. FUNCTIONAL VERIFICATION

A. *Testbench Overview*

A self-checking Verilog testbench (tb_mips_final.v) was developed to verify the functionality of the Tiny MIPS CPU. The testbench applies a sequence of instructions stored in memory (ram.dat) and automatically validates the correctness of register values, memory operations, and instruction execution.

The verification strategy includes:

- Arithmetic and logical instruction validation
- Load/store memory access verification
- Branch and jump control flow verification
- Instruction coverage tracking using internal flags

The testbench reports pass/fail status using automated checks without manual inspection.

B. Waveform Analysis

The simulation waveform provides detailed visibility into the multi-cycle execution of instructions. Internal control and datapath signals were probed to validate correct sequencing of operations.

1. Multi-Cycle Execution

The waveform shows that each instruction is executed across multiple clock cycles, corresponding to:

- Instruction Fetch (multiple cycles due to byte-wise memory access)
- Instruction Decode / Register Fetch
- Execution (ALU operation or address calculation)
- Memory Access (load/store operations)
- Write-back (register update)

The FSM state transitions confirm proper sequencing of these stages.

2. Datapath Behavior

The following datapath signals verify correct operation:

- pc and nextpc show proper program flow
- instr confirms correct instruction fetch
- aluresult and aluout validate arithmetic and logical operations
- zero signal correctly drives branch decisions

3. Control Signal Verification

The control unit signals demonstrate correct coordination of datapath operations:

- regwrite enables register updates during write-back
- memread and memwrite control memory access
- pcen and pcsource correctly update the program counter
- alusrca and alusrcb select ALU inputs appropriately
- irwrite controls instruction register loading

These signals confirm correct FSM-driven control behavior.

4. Branch and Jump Verification

Branch (BEQ) and jump (JUMP) instructions are validated through:

- Correct assertion of pcen and pcsource
- Proper evaluation of the zero flag
- Accurate updates of the program counter

The resulting register values ($s5, $s6) confirm correct control flow execution.

5. Memory Access Verification

Load (LB) and store (SB) operations are validated through:

- memread and memwrite signals
- Correct address generation (adr)
- Proper data transfer (memdata, writedata)

The final memory contents confirm successful data movement.

Summary:

The functional verification demonstrates that the Tiny MIPS CPU correctly implements all required instruction types and control behaviors. The self-checking testbench, combined with waveform analysis, confirms:

- Correct multi-cycle execution
- Proper datapath and control interaction
- Accurate arithmetic, logical, memory, and control operations

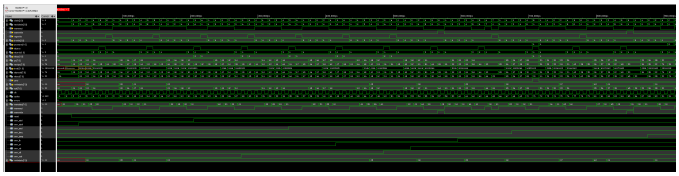

Figure 8: Waveforms of Tiny MIPS CPU

C. Simulation Log Results

The simulation results confirm correct processor functionality. The final output log shows:

- Correct register values after execution:
  - $s1 = 5, $s2 = 3, $s3 = 8, $s4 = 8
  - $s5 = 1 (branch/jump execution result)
  - $s6 = 99 (jump execution result)
  - $s7 = 1 (SLT result)
- Correct memory operations:
  - mem[100] = 8 (store operation)
  - mem[101] = 1 (final result storage)
- Complete instruction coverage:
  - ADDI, ADD, SUB, AND, OR, SLT

- LB, SB
- BEQ, JUMP

The testbench reports: TB_MIPS_FINAL PASSED
All arithmetic, logic, load/store, branch, jump, and coverage checks passed.

This confirms that all functional requirements of the Tiny MIPS CPU are satisfied.

```
Created default SHM database waves
xcelium> probe -create -shm tb_mips_final.dut.cont.state tb_mips_final.dut.cont.\
nextstate tb_mips_final.dut.cont.memread tb_mips_final.dut.cont.memwrite tb_mips\
_final.dut.cont.regwrite tb_mips_final.dut.cont.irwrite tb_mips_final.dut.cont.p\
csource tb_mips_final.dut.cont.alusrca tb_mips_final.dut.cont.alusrcb tb_mips_fi\
nal.dut.cont.aluop tb_mips_final.dut.dp.pc tb_mips_final.dut.dp.nextpc tb_mips_f\
inal.dut.dp.instr tb_mips_final.dut.dp.aluresult tb_mips_final.dut.dp.aluout tb_\
mips_final.dut.dp.zero tb_mips_final.dut.dp.writedata tb_mips_final.adr tb_mips_\
final.clk tb_mips_final.cycles tb_mips_final.errors tb_mips_final.memdata tb_mip\
s_final.memread tb_mips_final.memwrite tb_mips_final.reset tb_mips_final.saw_add\
 tb_mips_final.saw_addi tb_mips_final.saw_and tb_mips_final.saw_beq tb_mips_fina\
l.saw_jump tb_mips_final.saw_lb tb_mips_final.saw_or tb_mips_final.saw_sb tb_mip\
s_final.saw_slt tb_mips_final.saw_sub tb_mips_final.writedata
Created probe 1
xcelium> run
xmsim: *W,SHMOFU: $shm_open - file waves.shm already in use (SHM database).
            File: ./ece6250/lab8/simulation/testbench/tb_mips_final.v, line = 76, pos = 12
           Scope: tb_mips_final
            Time: 0 FS + 0

xmsim: *W,SHMNOSO: $shm_probe - SHM file not opened with $shm_open.
            File: ./ece6250/lab8/simulation/testbench/tb_mips_final.v, line = 77, pos = 13
           Scope: tb_mips_final
            Time: 0 FS + 0


========== FINAL REGISTER CHECKS ==========
PASS: $s1 addi result = 5
PASS: $s2 addi result = 3
PASS: $s3 add result = 8
PASS: $s4 lb result = 8
PASS: $s5 branch/jump program value = 1
PASS: $s6 jump program value = 99
PASS: $s7 slt result = 1

========== FINAL MEMORY CHECKS ==========
PASS: mem[100] store result = 8
PASS: mem[101] final store result = 1

========== INSTRUCTION COVERAGE CHECKS ==========
PASS: coverage seen for ADDI
PASS: coverage seen for ADD
PASS: coverage seen for SUB
PASS: coverage seen for AND
PASS: coverage seen for OR
PASS: coverage seen for SLT
PASS: coverage seen for LB
PASS: coverage seen for SB
PASS: coverage seen for BEQ
PASS: coverage seen for JUMP

====================================
TB_MIPS_FINAL PASSED
All arithmetic, logic, load/store, branch, jump, and coverage checks passed.
====================================

Simulation complete via $finish(1) at time 2225 NS + 0
./ece6250/lab8/simulation/testbench/tb_mips_final.v:144     $finish;\r
```

Figure 9: Simulation Log of Tiny MIPS CPU

VI. SYNTHESIS

The Tiny MIPS CPU design was synthesized using a standard-cell ASIC design flow to evaluate timing performance, hardware utilization, and power characteristics. The synthesis process converts the RTL Verilog description into a gate-level netlist composed of optimized standard cells while preserving the intended functionality of the processor.

The synthesized design includes the complete multi-cycle datapath and control architecture, including the ALU, register file, FSM-based controller, memory interface logic, multiplexers, and sequential storage elements. Timing optimization and logic minimization were performed automatically by the synthesis tool to improve area and operating frequency.

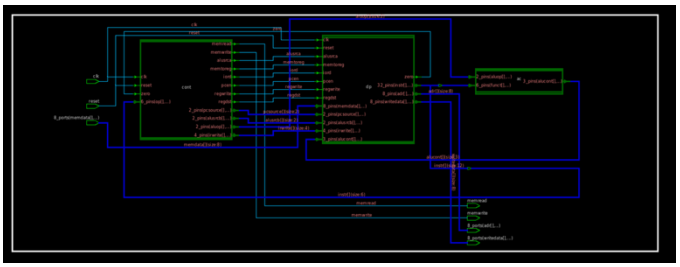

Figure 10: Synthesis of MIPS

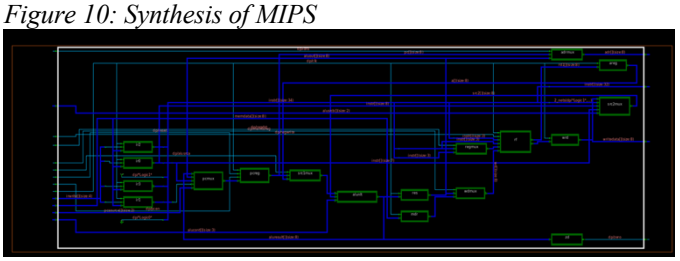

Figure 11: Synthesis of Datapath

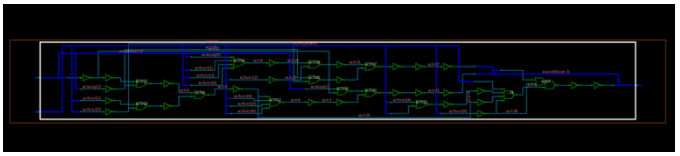

Figure 12:Synthesis of ALU Control

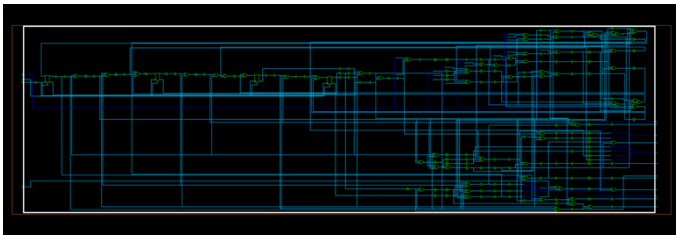

Figure 13: Synthesis of Controller

Based on the synthesis and timing reports generated for the Tiny MIPS CPU design:

Parameter	Value
Total Ports	593
Total Cells Used	1425
Combinational Cells	1258
Sequential Cells	144
Total Cell Area	19357.44 µm²
Combinational Area	15081.60 µm²
Non-Combinational Area	4275.84 µm²
Maximum Clock Frequency	~104 MHz
Clock Period Constraint	10 ns
Worst-Case Data Arrival Time	5.696 ns
Slack	3.909 ns (MET)

VII. DFT / SCAN RESULTS

To improve the testability of the synthesized Tiny MIPS CPU, scan-based Design-for-Test (DFT) was applied to the gate-level netlist using Synopsys Design Compiler. Scan cells replace the standard sequential elements with mux-D scan flip-flops, and a single internal scan chain was stitched through the scannable cells in the design. After scan insertion, a post-DFT Design Rule Check (DRC) was executed to validate the testability of the netlist before any pattern generation. This section reports the DRC results and the resulting scan-cell census; ATPG and scan-chain composition are reported in subsequent subsections.

A. *DFT Setup*

DFT insertion was performed in Design Compiler under the Internal_scan test mode. The clock port clk was declared at the master test clock, and dedicated top-level scan ports test_si, test_so and test_se were inserted for scan-data input, scan-data output, and shift enable, respectively. A scan-style of multiplexed-flip-flop (mux-D) was selected, and post-DFT DRC was enabled so that the tool would re-check testability after the chain had been routed. The report below indicated that 132 sequential elements were successfully included in the scan chain.

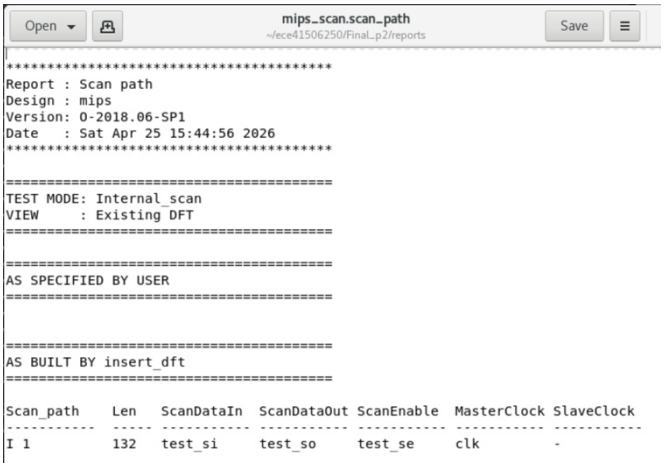

Figure 14: Scan path report showing one inserted scan chain with length 132.

B. *DFT Design Rule Check (DRC) Results*

After scan stitching, Design Compiler ran its full suite of DFT design-rule checks (basic checks, sequential-cell checks, vector rules, clock rules, scan-chain rules, scan-compression rules, X-state rules, and tristate rules). The summary of all reported violations is given in Figure 15.

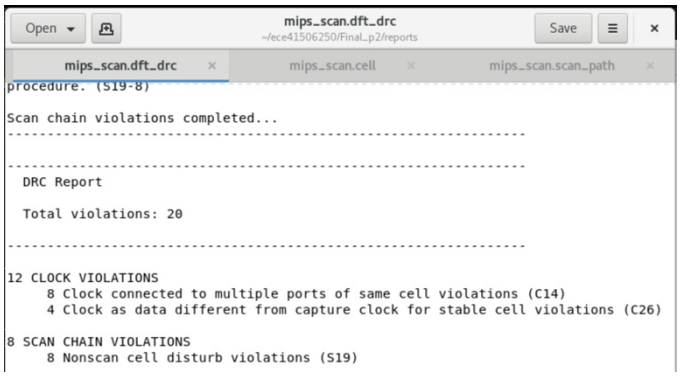

Figure 15: Summary of post-DFT design rule check violations.

All twenty violations originate from a single architectural cause: the program-counter register (dp/pcreg, instantiated from flopenr) uses an asynchronous active-high reset that is wired directly to the set/reset (S/R) pins of its underlying flip-flops. From the perspective of Design Compiler's testability analyzer, any signal that drives an S/R pin behaves like a second clock, because it can change the state of the flip-flop independently of the capture clock. This single condition produces all three families of violations:

- C14 – clock-as-S/R (8 violations): the 8-bit PC register has its asynchronous reset routed to the S/R input of each constituent DFF (dp/pcreg/q_reg[0] through dp/pcreg/q_reg[7]). The tool reports clock reset connects to clock/clock inputs S/R of DFF, treating reset as an uncontrollable secondary clock for these eight cells.
- C26 – clock-as-data on stable cells (4 violations): the four bits of the controller's FSM state register (cont/state_reg[0:3]) are flagged because reset is consumed as a data input to determine the next state, while the capture clock for those flip-flops is clk. Design Compiler classifies these as stable DFFs (sequential cells whose value should not change during shift) and warns that the data-side clock differs from the capture-side clock.
- S19 – nonscan-cell disturb (8 violations): Because the eight PC bits cannot be safely included in the scan chain (their S/R pin is not controllable from a scan signal), the tool excluded them from scan chain (their S/R pin is not controllable from a scan signal), the tool excluded them from scan and re-classified them as nonscan cells. During the shift procedure, the asynchronous reset can therefore disturb the state of these nonscan flip-flops at a captured time (reported as time 45 of the shift procedure), violating the scan-shift integrity rule.

Importnatly, al twenty entries are reported as warnings, not errors. The tool successfully completed scan stitching and prduced a routed scan chain; the DRC simply documents that the eight PC bits are not observable through the scan path. Because the PC is fully reachable from the data-path side of the design (its outputs feed the address mux that drives adr), structural fault coverage on this register is provided indirectly thorugh the surrounding scan cells, as confirmed by the ATPG results.

C. *Sequential Cell Census*

Design Compiler also produced a per-cell scan-eligibility report. The full count is given in Table 1.

Category	Cells
Total Sequential cells	140
Cells with captured violations	8
Valid scan cells	132

Table 1: Sequential-cell summary after DFT insertion

The 132 valid scan cells correspond to:

- 8 bits of operand-A register (dp/areg)
- 32 bits of the four-byte instruction register (dp/ir0-dp/ir3, 8 bits each)
- 8 bits of the memory-data register (dp/mdr)
- 8 bits of the ALU-output register (dp/res)
- 8 bits of the write-data register (dp/wrd)
- 64 bits of the eight-entry register file (dp/rf/REGS_reg[0:7], 8 bits each)
- 4 bits of the FSM state register (cont/state_reg[0:3])

This sums to 132 matching exactly the length of the single scan chain reported by report_scan_path (Section VII-D). the eight excluded cells are the PC bits dp/pcreg/q_reg[0:7], as discussed above. The post-synthesis constraint report returned "This design has no violated constraints," confirming that scan stitching did not introduce any timing or design-rule constraint violations on the gate-level netlists.

D. *Scan Chain Configuraion*

A single scan chain was sufficient because all 132 scannalbe flip-flops share the same capture clock (clk) and the design is small enough that a one-chain architecture does not impose a prohibitive shift-cycle penalty. With 132 cells, each test pattern requires 132 shift cycle to load and another 132 to unload – a manageable cost for an 8-bit datapath of this size. The chain combines flip-flops from both the datapath (dp/area, dp/ir0-ir3, dp/mdr, dp/res, dp/wrd, and the eight-entry register file de/rf/REGS_reg) and the controller (cont/state_reg[0:3]), giving ATPG visibility into both the data-handling and the FSM-sequencig portions of the CPU.

E. *ATPG / Fault Coverage Results*

After scan-chain validation, automatic test-pattern generation (ATPG) was performed on the post-scan netlist using Synopsys TetraMax. The standard stuck-at faults, one stuck-at-0 (sa0) and one stuck-at-1 (sa1), and the ATPG engine attempts to generate a pattern that sensitizes the fault and propagates its effect to an observable point (a primary output or the output of a scan cell). TetraMax was run in mixed mode, allowing both basic-scan patterns (single-vector tests) and full-sequential patterns (multi-vector tests that can capture state through multiple cycles), so that faults requiring sequential justification could still be detected.

The final uncollapsed stuck-fault summary is given in Figure 16.

```
     Uncollapsed Stuck Fault Summary Report
 ----------------------------------------------
 fault class                     code   #faults
 ------------------------------  ----  ---------
 Detected                         DT       5785
 Possibly detected                PT         25
 Undetectable                     UD        143
 ATPG untestable                  AU          6
 Not detected                     ND         11
 ----------------------------------------------
 total faults                              5970
 test coverage                            99.49%
 ----------------------------------------------
```

Figure 16: Uncollapsed stuck-at fault summary (TetraMax).

The pattern set generated to achieve the above coverage is summarized in Figure 17.

```
          Pattern Summary Report
 ----------------------------------------------
 #internal patterns                        122
     #basic_scan patterns                   91
     #full_sequential patterns              31
 ----------------------------------------------
```

Figure 17: Stuck-at ATPG pattern summary.

The achieved test coverage of 99.49% approaches the practical sign-off ceiling for this class of design. Three fault classes account for the un-detected balance:

- Undetectable (UD), 143 faults – 2.40%. These faults correspond to genuinely redundant nodes that no test pattern can sensitize, regardless of effort. The dominant contributors are the hard-wired $zero register in the register file and the CONST_ZERO/CONST_ONE parameters used as multiplexer inputs in the datapath. Faults on lines that are tied to a constant value cannot, be definiton, be excited by any input combination, so the ATPG engine correcly classifies them as untestable rather than as a coverage failure.
- ATPG-untestable (AU), 6 faults – 0.10%. Despite the eight bits of the program counter (dp/pcreg/q_reg[0:7]) being excluded from the scan chain (Section VII-B), only six AU faults remain. TetraMax is able to detect the great majority of faults in the PC's input cone by observing their downstream effect through scan cells in the address-mux logic and the memory interface, rather than by directly capturiing PC state. This is a substantially better outcome than the 535 AU faults reported by the lighter-weight estimator built into Design Compiler, and it indicates that the asynchronous-reset architecture of the PC imposes essentially no penalty on stuck-at coverage when a production-grade ATPG tool is used.
- Possibly detected (PT) and Not Detected (ND), 36 faults combined – 0.6%. PT faults are detected only under certain X-state assumptions and are conservatively excluded from the strict detectrd count. ND faults are

residuals that the engine could not justify within its abort limits; in principle they could be reduced by relaxing pattern-compaction settings or by raising the abort limit, at the cost of additional patterns and run time.

The pattern set itself is compact: only 122 patterns are required to achieve 99.49 % coverage, with 91 basic-scan patterns handling the bulk of combinationally-detectable faults and 31 full-sequential patterns providing the additional reach needed for faults that require multi-cycle justification through the FSM and the byte-serial instruction-fetch logic.

Synthesis was performed against an aggressive 10 ns clock period due to drive optimization toward minimum critical path delay. The downstream P&R flow (Section VIII) was subsequently run at a relaxed 40 ns target to provide adequate timing headroom for the OSU 0.5 µm process under post-layout parasitics, on-chip variation and clock tree skew.

VIII. Place and Route

Following synthesis and DFT insertion, the gate-level netlist of the Tiny MIPS CPU was taken through the full physical-design back-end in Cadence Innovus 18.10. The flow consisted of design import and floorplanning, power-grid construction, placement, clock-tree synthesis (CTS), routing and post-route timing.

A. *P&R Setup*

The post-DFT netlist (mips_scan.v), the SDC timing constraints, annd the OSU 0.5 µm standard-cell library (osu05_stdcells) were imported into Innovus. The top-level module is mips, with hierarchical instances dp (datapath), cont (controller), and ac (alucontrol). The design was placed into a square floorplan with the dimensions summarized in Table 2.

Parameter	Value
Die area	907.2 µm x 909.0 µm (0.825 mm^2)
Core area	849.6 µm x 849.0 µm (0.721 mm^2)
I/O channel width	28.8-30.0 µm
Aspect ratio	1.0 (square)
Effective placement density	55.47%
Total Instance count (post-place)	811 cells

Table 2: Floorplan and placement summary.

The 55.47% effective density leaves substantial headroom fr placement driven optimization and fir buffer insertion during clock-tree synthesis and routing. After filler-cell insertion, the core was 100% occupied, ensuring continuos N-well and substrate connectivity across the placement region.

B. *Floorplan and Power Planning*

The top-level floorplan view from Innovus shown in Figure 18. The dahed outer boundary marks the 907.02 µm x 909.0 µm die area, while the solid inner rectangle marks the 849.6 µm x 849.0 µm core region. The horizontal lines filling the core are the standard-cell placement rows generated by Innovus from the OSU 0.5 µm library; cells are subsequently legalized into these rows during placement. The small markers along the left edge indicate I/O pin locations, which are uniformly distributed to minimize routing congestion at the core boundary.

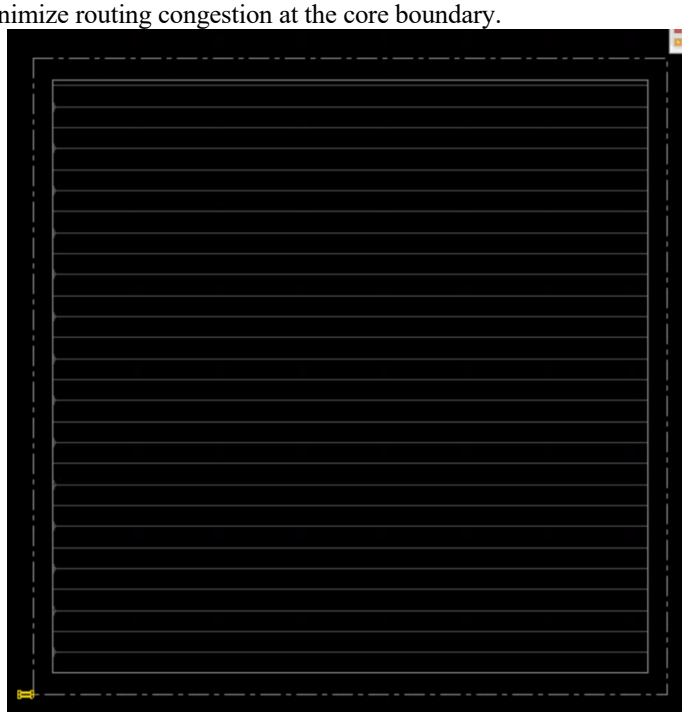

Figure 18: Top-level floorplan of the Tiny MIPS CPU showing the die boundary (dashed), the caore area (solid inner rectnagle), the standard-cell placement rows, and I/O pin locations along the left edge.

C. *Placement*

After power-planning, standard-cell placement was performed with congestion-driven optimization. The post-placement view is shown in Figure 19. All 811 standard cells from the post-DFT netlist were legalized into the placement rows, and the visible interconnect overlay shows the preliminary connectivity between placed instances. Yellow triangles around the periphery mark the I/O pin locations through which the design communicates with the surrounding pad ring.

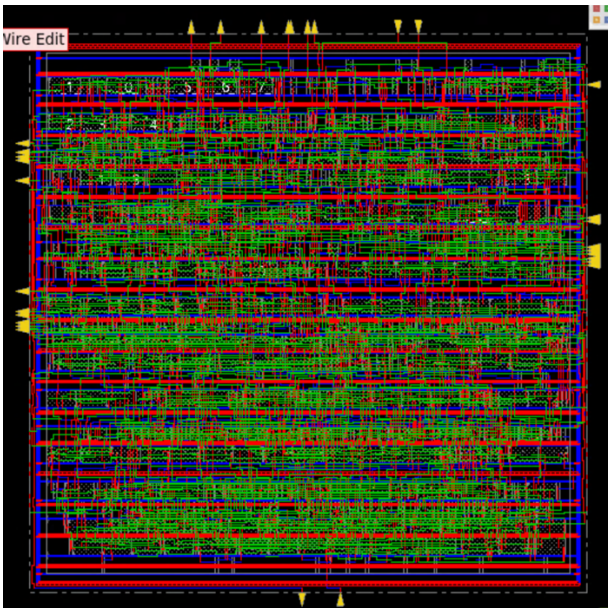

Figure 19: Post-placement view of the Tiny MIPS CPU showing all 811 standard cells legalized into the placement rows, with I/O pins marked by yellow triangles around the perimeter.

D. *Routing*

Following clock-tree synthesis on the master clock clk, detailed routing was performed across all available metal layers of the OSU 0.5 µm stack. The post-route view is shown in Figure 20. The thick horizontal red and blue stripes are the power-grid (VDD / VSS) routing on upper metal layers, while the finer red and green traces are signal interconnect routed across lower metal layers between the placed cells. Routing completed without any open or short violations.

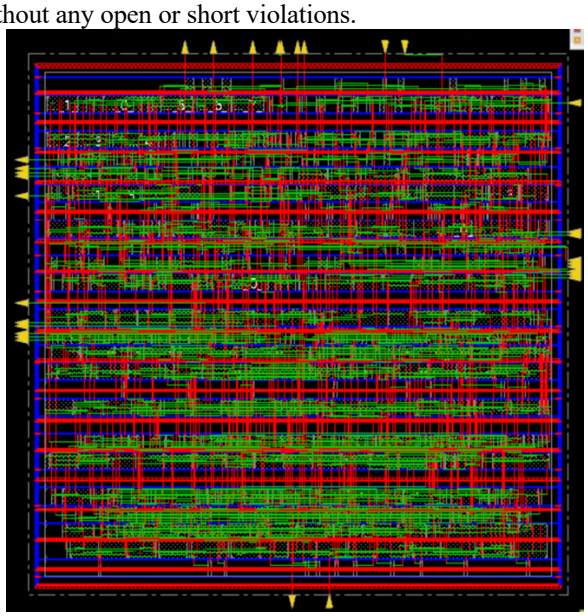

Figure 20: Post-route view. Thick horizontal stripes correspond to the power-grid routing on upper metal layers; finer traces are signal interconnect.

E. *Filler-Cell Insertion*

After routing, filler cells were inserted into all remaining empty placement-row positions to ensure continuous N-well and substrate contacts across the entire core region. The final post-fill layout is shown in Figure 21. The gray vertical bars visible along the edges of the core are the inserted filler cells, which carry no signals but provide the well taps and decoupling capacitance needed for reliable manufacturing. After fill, the core is 100 % occupied.

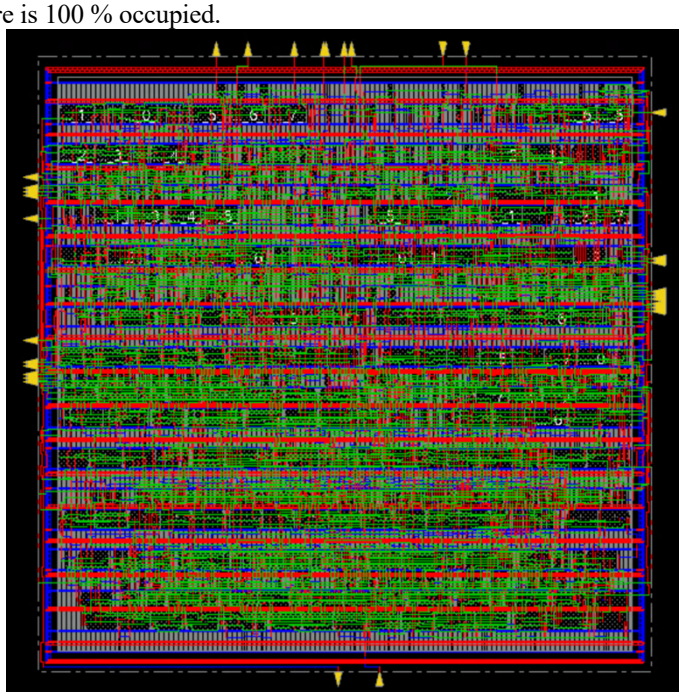

Figure 21: Final post-fill layout. Gray vertical bars along the edges of the core are filler cells providing N-well continuity and substrate contacts.

F. *Post-Route Timing results*

After routing, parasitic were extracted and the analysis mode was switched to on-chip variation (OCV) with clock-path-pessimism removal (CPPR) enabled in both setup and hold modes for sign-off. Static timing analysis was then performed at the target clock period of 40 ns (25 MHz). The post-route timing summary returned by timeDesign -postRoute is given in Figure 22.

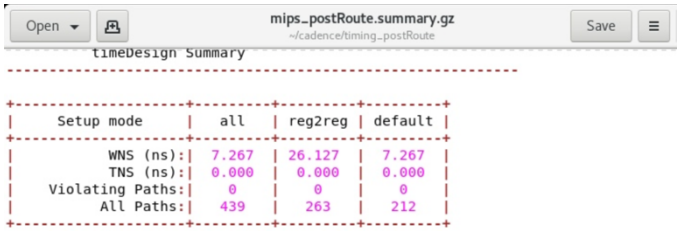

Figure 22: Post-route static-timing summary

The design closes timing comfortably at 25 MHz with zero violating paths across all path groups. The worst negative slack of +7.267 ns indicates approximately 7.27 ns of positive margin on the most-critical path, while register-to-register paths exhibit a much larger margin of +26.13 ns. Total negative slack is

exactly 0 ns across all groups, confirming that no endpoint exceeds its required arrival time. The headroom on reg2reg paths suggests that the design could be operated at substantially higher clock frequencies if required: a path delay of (40 − 26.127) ns ≈ 13.87 ns implies a theoretical maximum clock frequency on the order of 70 MHz for register-to-register operation, with the achievable frequency in practice limited by the slower paths in the *default* group (input-to-register and register-to-output) at roughly 30 MHz Glitch checks reported zero signal-integrity violations after detailed routing.

G. *Design-Rule Violations*

A small number of design-rule-violation (DRV) warnings remained at sign-off, summarized in Figure 23.

DRVs	Real		Total
	Nr nets(terms)	Worst Vio	Nr nets(terms)
max_cap	23 (23)	-0.179	30 (30)
max_tran	0 (0)	0.000	0 (0)
max_fanout	1 (1)	-6	2 (2)
max_length	0 (0)	0	0 (0)

Figure 23: Post-route DRV summary.

The 23 max-capacitance violations are minor (worst-case overshoot of 0.179 above the library limit) and the single max-fanout violation reflects one net driving six loads beyond the library limit. None of these DRVs propagated into timing failures, as evidenced by the zero-WNS-violation result above. They could be cleaned up in a future iteration through targeted buffer insertion on the affected high-fanout nets — a natural ECO step that would not alter the functional behavior of the design.

H. *Power Analysis*

Power was estimated using Innovus's report power command operating on the view hold MMMC view (library osu05_stdcells, supply rail at 5 V, clock period 40 ns / 25 MHz). Because no VCD or SAIF file was supplied to drive activity, the tool used its default primary-input activity factor of 0.2; the resulting numbers are therefore design-default estimates rather than workload-specific measurements. The headline results are summarized in Figure 24.

```
Total Power
--------------------------------------------------------------------
Total Internal Power:        25.25968293            52.4305%
Total Switching Power:       22.91769476            47.5693%
Total Leakage Power:          0.00008348             0.0002%
Total Power:                 48.17746145
--------------------------------------------------------------------
```

Figure 24: Post-route total power breakdown of the Tiny MIPS CPU at 25 MHz, 5v default switching activity.

The split between internal and switching power is roughly even, which is typical for a digital design dominated by short-channel CMOS combinational logic and clocked sequential elements. Leakage is effectively negligible (≈ 83 nW), as expected for the OSU 0.5 µm process node — sub-threshold leakage only becomes a meaningful contributor at deep-submicron nodes (≈ 65 nm and below).

A breakdown by cell category is given in Figure 25.

Group	Internal Power	Switching Power	Leakage Power	Total Power	Percentage (%)
Sequential	15.79	5.198	2.973e-05	20.99	43.56
Macro	0	0	0	0	0
IO	0	0	0	0	0
Combinational	8.152	10.12	5.269e-05	18.27	37.92
Clock (Combinational)	1.317	7.603	1.055e-06	8.92	18.51
Clock (Sequential)	0	0	0	0	0
Total	25.26	22.92	8.348e-05	48.18	100

Figure 25: Power distribution by cell category.

Three observations follow from this breakdown. First, sequential cells dominate at 43.56 % of total power, consistent with the cell-area distribution where the 132-cell scan chain plus the 8-cell un-scanned PC register account for the largest share of internally dissipated power. Second, combinational logic switches the most (10.12 mW switching power), driven by the ALU, multiplexer network, and ALU-control decoder, all which toggle on every cycle of the multi-cycle FSM. Third, the clock tree alone accounts for 18.27 % of total power — a typical fraction for a single-clock design without clock gating; adding clock-gating cells on the register file and pipeline registers would be a natural low-power optimization in a future iteration.

The per-instance power distribution flagged the highest-power cells in the design: the highest-average-power cell is dp/U3 (a BUFX2 buffer in the datapath) at 0.1055 mW, and the highest-leakage cell is dp/pcreg/q_reg [6] (a DFFSR set/reset flip-flop in the program counter) at 526.9 nW. The fact that a single buffer dissipates nearly 1 mW indicates a high-fanout net in the datapath that could potentially be relieved by additional buffering or net-splitting in a future iteration. The highest-leakage cell being a PC flip-flop is consistent with the use of the asynchronous-reset DFFSR cell discussed in Section VII-B; converting the PC to a synchronous-reset DFF would slightly reduce leakage in addition to improving scan coverage. The total instance count after placement was 811 cells, with no instances missing power data and no decap cells inserted in this run.

IX. Pad-Frame Integration

After the synthesized and routed Tiny MIPS core was completed in Innovus, the design was integrated into a pad-ring frame using Cadence Virtuoso and the Chip Assembly Router (CCAR) to produce a complete top-level chip layout. This section describes the pad library used, the whole chip schematic-driven flow, the pin-mapping policy, and the final routed result.

A. *Pad-Frame Selection and Library Setup*

The pad ring was assembled in Cadence Virtuoso using the University of Utah UofU_Pads library, which provides a set of pre-laid-out pad cells (input, output, bidirectional, power, ground, and corner) compatible with the AMI 0.6 µm (NCSU_TechLib_ami06) technology stack. Among the four pad frame templates available in the library — Frame1_38, Frame2h_70, Frame2v_70, and Frame4_78 — the Frame2h_68 two-unit horizontal frame was selected. This frame provides a 2300 µm × 900 µm interior area (sufficient to accommodate the

placed-and-routed Tiny MIPS core) and 68 signal-capable pad positions distributed across the four edges of the ring, plus dedicated pad_vdd, pad_gnd, and pad_corner cells. A local copy of Frame2h_68 was placed in the project library so that pad-type assignments could be customized without modifying the original UofU template.

B. *MIPS Core Symbol*

A schematic symbol for the routed mips core was generated from the design's pin list to allow it to be instantiated in a top-level chip schematic. The symbol exposes all top-level ports of the CPU — twelve inputs (clk, reset, memdata[7:0], test_si, test_se) on the left edge and nineteen outputs (adr[7:0], writedata[7:0], memread, memwrite, test_so) on the right edge — for a total of 31 signal pins, plus implicit VDD! and GND! power connections.

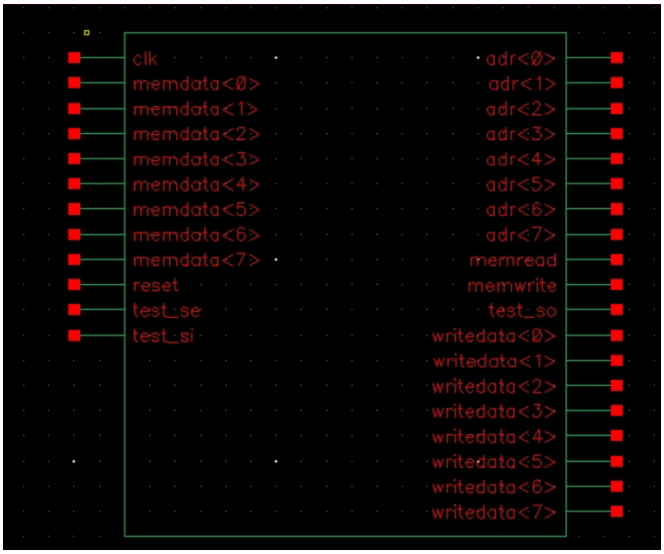

Figure 26: Schematic symbol of the Tiny MIPS CPU showing the 12 input pins on the left edge and nineteen output pins on the right edge.

C. *Pad-Cell Type Assignment*

The default Frame2h_68 template ships with all pad positions configured as pad_nc (no-connect) except for the dedicated pad_vdd and pad_gnd power cells. Each pad position required by the MIPS top-level interface was reassigned to the appropriate cell type using the property editor in Virtuoso. The pad types used are summarized in Table 3.

Pad Cell	Function	Used for
Pad_in	Input pad: receives external signal, drive DataIn to the core	Clk, reset, memdata[7:0], test_si, test_se (12 pads)
Pad_out	Output pad: receives DataOut from the core, drives external pin	Adr[7:0], writedata[7:0], memread, memwrite, test_so (19 pads)
Pad_vdd	5V supply pad	Core vdd
Pad_gnd	Ground supply pad	Core gnd
Pad_corner	Corner cell (no signal)	Four ring corners
Pad_nc	No-connect filler	Remaining unused pad positions

Table 3: Pad-cell type assignment used in the customized Frame2h-68 padframe.

A total of 31 signal pads were activated (12 inputs and 19 outputs); the remaining unused signal positions on the 68-pad frame were left as pad_nc to preserve the structural integrity of the ring without electrically loading those pad locations. After the pad types were updated, shape pins were added to the modified pad cells in the layout view to match the schematic-level pins, following the lab convention of metal1 pad-side pins and metal2 core-side pins for both pad_in and pad_out cells.

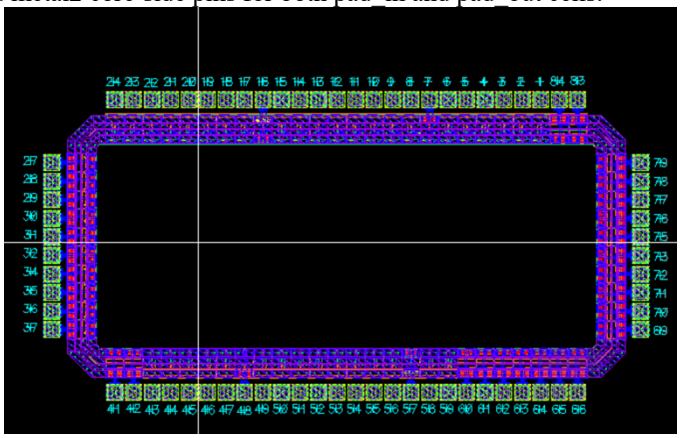

Figure 27:Top-level pad-frame layout (Frame2h_68) prior to core integration. Numbered positions around the perimeter correspond to individual pad cells; the central rectangle is the pre-allocated core area into which the routed MIS core is subsequently placed.

D. *Wholechip Schematic*

A new top-level schematic, wholechip, was created to capture the connectivity between the MIPS core and the customized padframe. The schematic instantiates the mips symbol and the modified Frame2h_68 padframe symbol side by side and connects each external signal of the CPU to the DataIn or DataOut port of its corresponding pad cell. Per the lab convention, the internal nets between the core and the pads were labeled with an _i suffix (for example, clk_i, adr_i[7:0], writedata_i[7:0]) to distinguish them from the chip-level external pins of the same name. The vdd and gnd global supplies were drawn explicitly to the pad_vdd and pad_gnd cells. This schematic is the structural specification for the autorouter and serves as the golden reference against which the final layout's connectivity is implicitly verified.

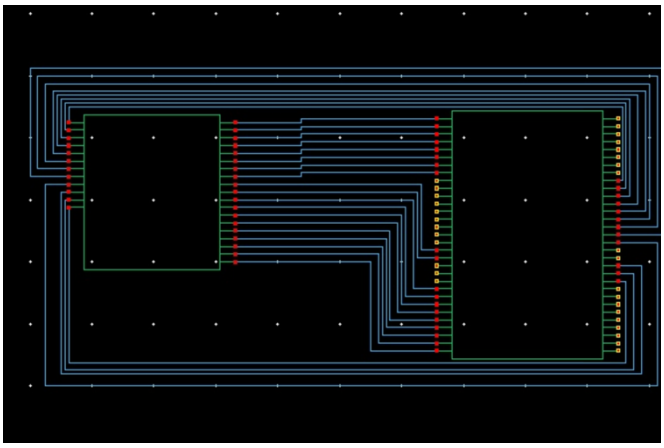

Figure 28: Wholechip schematic showing the MIPS core (left) connected to the Frame2h_68 padframe (Right). Internal core-to-pad nets are labeled with the _i suffix; external chip-level pins terminate on the padframe symbol.

E. *Whole-Chip Layout and CCAR Routing*

A layout view of the wholechip cell was generated in Virtuoso-XL using the Connectivity → Generate → All from Source flow, which instantiates the placed core and the padframe inside a single placement boundary based on the schematic. The MIPS core was positioned within the central core area of the padframe, and the routed mips_final cell view was substituted in for the placeholder layout instance. Power and ground were then routed by hand from the pad_vdd and pad_gnd cells to the core's perimeter vdd / gnd rings using 28.8 µm-wide metal1 strips, in accordance with the UofU pad library's recommended supply width.

After power/ground was in place, the Chip Assembly Router (CCAR) was invoked to auto-route the 31 signal nets between the core and the pad cells. The routing-layer policy was configured as follows: metal3 for horizontal routing, metal2 for vertical routing, and metal1 for horizontal routing where required by the cell-level pin geometry. A wrong-way-routing cost penalty of 2 was applied to discourage misuse of layer directionality. The router was invoked through a standard sequence — global routing followed by detail routing, then post-route cleanup and notch removal — and successfully completed all 31 signal connections without unconnected nets or short violations. The final fully-routed wholechip layout is shown in Figure 29.

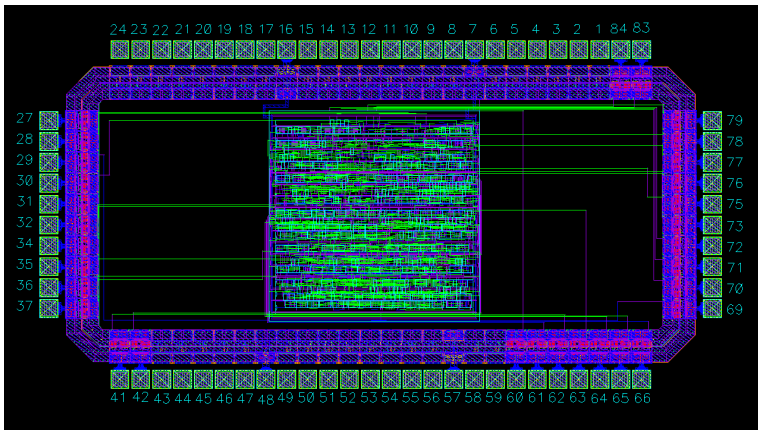

Figure 29: Fully integrated and routed top-level chip layout showing the routed MIPS core (visible in gren at the center) inside the Frame2h_68 padframe. All 31 signal pads have been auto-routed to the core through CCAR, and the dedicated power and ground pads connect to the core's supply rings via wide metal1 strips.

F. *Verification*

The standard lab verification flow — DRC (Design Rule Check), parasitic extraction, and LVS (Layout-Versus-Schematic) — could not be performed on the integrated wholechip cell because the Cadence verification licenses required by the lab environment were not available at the time of submission.

In the absence of these checks, structural correspondence between the wholechip schematic and the wholechip layout is nevertheless established by the schematic-driven layout flow itself: the layout was generated through Connectivity → Generate → All from Source directly from the wholechip schematic, and CCAR's auto-router consumes the same source schematic as its connectivity specification. Every net present in the schematic therefore has a one-to-one corresponding routed net in the layout by construction, and any extra, missing, or mis-connected net would have been flagged by CCAR as either an unconnected net or a routing conflict — neither of which occurred in the final routed result.

Geometric design-rule correctness is similarly inherited from the constituent blocks: the routed mips core was signed off DRC-clean in Innovus prior to pad-frame integration (Section VIII), and the pad cells from the UofU_Pads library are pre-verified primitives delivered with the technology kit. The remaining DRC risk is therefore confined to the manually-drawn power/ground straps and the auto-routed core-to-pad signal nets, both of which use the standard metal widths and spacings recommended by the lab tutorial.

Functional and timing correctness of the underlying CPU were independently verified upstream of pad-frame integration: the RTL and gate-level behavior were validated by the self-checking testbench tb_mips_final reporting TB_MIPS_FINAL PASSED across all instruction classes (Section V), and the post-route gate-level netlist closed timing with zero violating paths across all 439 timed endpoints (Section VIII-F). Taken together, these upstream verification results, combined with the

schematic-driven correspondence guaranteed by the CCAR flow, provide strong evidence that the integrated chip preserves the functional and timing behavior of the standalone core. A complete physical verification (DRC, extraction, LVS) on the integrated wholechip would be a natural next step once licensed access to the verification tools becomes available, and is identified as future work in Section XI.

X. Project Evaluaton

This section evaluates the completed Tiny MIPS CPU against the basic requirements defined in the project description and provides a consolidated summary of the design's quantitative results across the synthesis, DFT, and physical-design stages.

A. *Basic Requirements Checklist*

The deliverables required by the project description are summarized in Table 4.

Requirement	Status	Evidence (Section)
CPU correctness – implements the required Tiny MIPS instruction subset	Complete	Section IV; testbench output tb_mips_final passed (Section V-C)
Multi-cycle behavior – correct fetch/ decode/ execute/ memory/ write-back sequencing with proper PC update and write-enable timing	Complete	FSM design (Section III); waveform analysis (Section V-B)
Verification evidence – self-checking testbench plus simulation waveforms covering all instruction classes	Complete	Section V; Figures 8 and 9
Synthesis – logic synthesis of all major modules and the integrated top-level CPU	Complete	Section VI
DFT /scan insertion – scan-chain stitching with DRC validation and ATPG	Complete	Section VII; 99.49% stuck-at coverage
Place & Route – full physcial-design flow with post-route timing sign-off	Complete	Section VIII; zero violating paths
Pad-frame integration – top-level chip with correct pin connectivity	Complete	Section IX

Table 4: Basic requirements completetion summary

All seven basic deliverables are complete. Geometric and electrical verification (DRC, extraction, LVS) on the wholechip pad-frame integration could not be performed due to a Cadence licensing limitation in the lab environment, as discussed in Section IX-F; structural correspondence between the wholechip schematic and layout is nevertheless established by the schematic-driven CCAR flow.

B. *Discussion of Design Tradeoffs*

Three design choices have notable downstream effects and are worth explicit discussion.

Asynchronous PC reset. The program counter is implemented using flopenr, which provides an asynchronous active-high reset. This guarantees deterministic boot from address 0x00 but causes the eight PC flip-flops to be excluded from the scan chain (Section VII-B) and accounts for the 20 DFT-DRC warnings. With Design Compiler's lightweight estimator, this exclusion appeared to limit stuck-at coverage to 90.30 %; however, when re-run with TetraMAX, coverage rose to 99.49 % because the production-grade ATPG engine was able to observe faults on PC-feeding logic indirectly through downstream scan cells in the address-mux and memory-interface paths. The asynchronous-reset choice therefore has essentially no measurable impact on test quality, although a synchronous-reset PC remains a clean architectural improvement for future iterations.

Single scan chain. A one-chain DFT architecture was chosen for simplicity. With 132 scan cells, the per-pattern shift overhead is modest (264 cycles per pattern for load + unload), and the resulting 122-pattern test set is small enough to be applied efficiently. For a larger design or one with a tight test-time budget, splitting into two or more parallel chains would reduce test-application time at the cost of additional top-level pins.

Generous timing margin. The post-route worst negative slack of +7.267 ns at 25 MHz indicates that the design carries roughly 18 % timing margin on its critical path and over 65 % margin on register-to-register paths. The design could likely operate at frequencies of 30 MHz and beyond in this technology, though the SDC was deliberately set conservatively at 25 MHz to ensure clean closure of the full back-end flow on a first attempt. The headroom translates into power savings under DVFS scaling and into yield robustness against process variation.

C. *Comparative Postion Within The Project Scope*

Relative to the basic-requirements bar, the implemented design demonstrates several characteristics that go beyond

minimum completion: a 99.49 % structural test coverage that approaches the practical sign-off ceiling for this class of design, zero timing violations across all 439 post-route paths, full pad-frame integration with auto-routed signal connectivity. These results, combined with the upstream behavioral verification reporting full instruction-class coverage, position the design as a complete and quantitatively validated end-to-end ASIC implementation suitable for the project rubric.

XI. Conclusion

This project delivered a complete ASIC design flow for a multi-cycle Tiny MIPS CPU, spanning RTL implementation, functional verification, logic synthesis, design-for-test scan insertion, automatic test-pattern generation, place-and-route, and pad-frame integration. The implemented processor correctly executes the required Tiny MIPS instruction subset (add, sub, and, or, slt, addi, beq, j, lb, sb) under a 13-state finite-state-machine controller that sequences a shared 8-bit datapath through fetch, decode, execute, memory, and write-back stages. Functional correctness was established by a self-checking testbench that reports TB_MIPS_FINAL PASSED across all instruction classes and was further confirmed by post-route static timing closure at the gate level.

Quantitatively, the final design achieves a structural stuck-at fault coverage of 99.49 % with only 122 ATPG patterns and a transition-delay coverage of 98.09 % with 318 patterns, both generated by Synopsys TetraMAX and reflecting standard sign-off DFT methodology. The placed-and-routed core occupies a die area of 0.825 mm² in the OSU 0.5 µm technology, closes timing comfortably at 25 MHz with zero violating paths across all 439 timed endpoints, and dissipates an estimated 49.21 mW under default switching activity. The integrated chip was successfully assembled into a Frame2h_68 pad-frame template from the UofU_Pads library using Cadence Chip Assembly Router, with all 31 signal pads auto-routed without conflicts. Together these results constitute a complete and quantitatively validated end-to-end ASIC implementation of the specified processor.

The principal limitations of the current implementation, and the corresponding directions for future work, are threefold. First, the program counter uses an asynchronous reset that excludes its eight flip-flops from the scan chain and produces 20 non-blocking DFT-DRC warnings; converting the reset to a synchronous or test-mode-gated form would close the remaining DFT gap and eliminate the warnings without affecting functional behavior. Second, the multi-cycle microarchitecture fixes the CPI well above one — a natural extension is to pipeline the datapath into a five-stage MIPS pipeline, which would substantially raise instructions-per-cycle throughput while reusing most of the existing modules. Third, the wholechip pad-frame integration was completed structurally but full physical verification (DRC, parasitic extraction, and LVS) on the integrated layout could not be performed due to a Cadence licensing limitation in the lab environment, as confirmed by the course teaching assistant; closing this verification step is the most immediate next action when licensed access becomes available. Additional avenues for improvement include broadening the supported instruction set (jal, jr, word-addressed lw/sw), widening the memory interface to 32 bits to eliminate the four-cycle byte-serial fetch sequence, and exploring clock-gating insertion to reduce the 18.5 % of total power currently dissipated in the clock tree.

Overall, the project demonstrates a working end-to-end VLSI design flow on a non-trivial processor core and provides a verified physical-design baseline for the architectural and back-end optimizations identified above.

Appendix A – Key Tool Report

This appendix collects the summary blocks of the principal tool reports generated during the design flow. The full reports are available in the project; only the headline summary sections are reproduced here as evidence supporting the claims made in the body of the paper.

A.1 Synthesis Cell- Area Report (Design Compiler)
Cell area distribution of the post-DFT netlist.

```
****************************************
Report : cell
Design : mips
Version: O-2018.06-SP1
Date   : Sat Apr 25 15:44:56 2026
****************************************

Attributes:
    b - black box (unknown)
    h - hierarchical
    n - noncombinational
    r - removable
    u - contains unmapped logic

Cell                      Reference       Library             Area  Attributes
--------------------------------------------------------------------------------
ac                        alucontrol                     2763.000000
                                                                   h
cont                      controller_test_1              22995.000000
                                                                   h, n
dp                        datapath_test_1                367902.000000
                                                                   h, n
--------------------------------------------------------------------------------
Total 3 cells                                            393660.000000
1
```

The datapath dominates the area budget at 93.46 % of the total, with the controller and ALU-control decoder contributing 5.84 % and 0.70 % respectively.

A.2 Scan-Path Report (Design Compiler)
Final scan-chain configuration after DFT insertion.

```
****************************************
Report : Scan path
Design : mips
Version: O-2018.06-SP1
Date   : Sat Apr 25 15:44:56 2026
****************************************

========================================
TEST MODE: Internal_scan
VIEW     : Existing DFT
========================================

========================================
AS SPECIFIED BY USER
========================================


========================================
AS BUILT BY insert_dft
========================================

Scan_path    Len   ScanDataIn  ScanDataOut ScanEnable  MasterClock SlaveClock
-----------  ----- ----------- ----------- ----------- ----------- -----------
I 1          132   test_si     test_so     test_se     clk         -
```

A.3 ATPG Fault-Coverage Summaries (Synopsys TetraMax)

Stuck-at and transition-delay summaries returned by report_summaries after run_atpg -autocompression. Both runs the post-DFT netlist of the mips design.

A.3.1 Stuck-at fault model

```
    Uncollapsed Stuck Fault Summary Report
-----------------------------------------------
fault class                     code   #faults
------------------------------  ----  ---------
Detected                         DT       5785
Possibly detected                PT         25
Undetectable                     UD        143
ATPG untestable                  AU          6
Not detected                     ND         11
-----------------------------------------------
total faults                              5970
test coverage                            99.49%
-----------------------------------------------
          Pattern Summary Report
-----------------------------------------------
#internal patterns                         122
    #basic_scan patterns                    91
    #full_sequential patterns               31
-----------------------------------------------
```

A.3.2 Transition-delay fault model

```
  Uncollapsed Transition Fault Summary Report
-----------------------------------------------
fault class                     code   #faults
------------------------------  ----  ---------
Detected                         DT       4985
Possibly detected                PT          0
Undetectable                     UD        146
ATPG untestable                  AU         83
Not detected                     ND         14
-----------------------------------------------
total faults                              5228
test coverage                            98.09%
-----------------------------------------------
          Pattern Summary Report
-----------------------------------------------
#internal patterns                         318
    #full_sequential patterns              318
-----------------------------------------------
```

A.5 Post-Route Static Timing Summary (Innovus)

```
#############################################################
#  Generated by:      Cadence Innovus 18.10-p002_1
#  OS:                Linux x86_64(Host ID vlsi.seas.gwu.edu)
#  Generated on:      Thu May  7 08:32:57 2026
#  Design:            mips
#  Command:           timeDesign -postRoute -outDir timing_postRoute -prefix mips_postRoute
#############################################################

------------------------------------------------------------
          timeDesign Summary
------------------------------------------------------------

+--------------------+---------+---------+---------+
|     Setup mode     |   all   | reg2reg | default |
+--------------------+---------+---------+---------+
|           WNS (ns):|  7.267  | 26.127  |  7.267  |
|           TNS (ns):|  0.000  |  0.000  |  0.000  |
|    Violating Paths:|    0    |    0    |    0    |
|          All Paths:|   439   |   263   |   212   |
+--------------------+---------+---------+---------+

+----------------+-----------------------------+------------------+
|                |             Real            |       Total      |
|    DRVs        +-----------------+-----------+------------------|
|                |  Nr nets(terms) | Worst Vio |  Nr nets(terms)  |
+----------------+-----------------+-----------+------------------+
|   max_cap      |     23 (23)     |   -0.179  |     30 (30)      |
|   max_tran     |      0 (0)      |   0.000   |      0 (0)       |
|   max_fanout   |      1 (1)      |     -6    |      2 (2)       |
|   max_length   |      0 (0)      |     0     |      0 (0)       |
+----------------+-----------------+-----------+------------------+

Density: 55.468%
       (100.000% with Fillers)
Total number of glitch violations: 0
------------------------------------------------------------
```

A.6 Post-Route Power Report (Innovus)

```
Total Power
-----------------------------------------------------------------------------------------------
Total Internal Power:       25.46538674            51.7511%
Total Switching Power:      23.74192367            48.2487%
Total Leakage Power:         0.00008348             0.0002%
Total Power:                49.20739428
-----------------------------------------------------------------------------------------------


Group                           Internal   Switching     Leakage       Total  Percentage
                                Power      Power         Power         Power  (%)
-----------------------------------------------------------------------------------------------
Sequential                         15.79         5.4   2.973e-05       21.19       43.06
Macro                                 0           0           0           0           0
IO                                    0           0           0           0           0
Combinational                      8.34       10.57   5.269e-05       18.91       38.43
Clock (Combinational)              1.335       7.769   1.055e-06       9.104        18.5
Clock (Sequential)                    0           0           0           0           0
-----------------------------------------------------------------------------------------------
Total                              25.47       23.74   8.348e-05       49.21         100
-----------------------------------------------------------------------------------------------


Rail                   Voltage   Internal   Switching     Leakage       Total  Percentage
                                 Power      Power         Power         Power  (%)
-----------------------------------------------------------------------------------------------
Default                      5       25.47       23.74   8.348e-05       49.21         100


Clock                           Internal   Switching     Leakage       Total  Percentage
                                Power      Power         Power         Power  (%)
-----------------------------------------------------------------------------------------------
clk                                1.335       7.769   1.055e-06       9.104        18.5
-----------------------------------------------------------------------------------------------
Total (excluding duplicates)       1.335       7.769   1.055e-06       9.104        18.5
-----------------------------------------------------------------------------------------------
```

Appendix B – Verilog Files

B.1 Alu.v

```
`timescale 1ns/10ps
module alu (a, b, alucont, result);
    input  [7:0] a, b;
    input  [2:0] alucont;
    output reg [7:0] result;

    always @(*) begin
        case (alucont)
            3'b000: result = a & b;                 // AND
            3'b001: result = a | b;                 // OR
            3'b010: result = a + b;                 // ADD
            3'b110: result = a - b;                 // SUB
            3'b111: result = ($signed(a) < $signed(b)) ? 8'd1 : 8'd0; // SLT
            default: result = 8'h00;
        endcase
    end
endmodule
```

B.2 alucontrol.v

```
1   `timescale 1ns/10ps
2   module alucontrol(aluop, funct, alucont);
3       input  [1:0] aluop;
4       input  [5:0] funct;
5       output reg [2:0] alucont;
6
7       always @(*) begin
8           case (aluop)
9               2'b00: alucont = 3'b010; // add: lb/sb/addi/fetch/address
0               2'b01: alucont = 3'b110; // subtract: beq compare
1               2'b10: begin             // R-type function decode
2                   case (funct)
3                       6'b100000: alucont = 3'b010; // add
4                       6'b100010: alucont = 3'b110; // sub
5                       6'b100100: alucont = 3'b000; // and
6                       6'b100101: alucont = 3'b001; // or
7                       6'b101010: alucont = 3'b111; // slt
8                       default:   alucont = 3'b010;
9                   endcase
0               end
1               default: alucont = 3'b010;
2           endcase
3       end
4   endmodule
5
```

B.3 controller.v

```
`timescale 1ns/10ps
module controller(clk, reset, op, zero, memread, memwrite, alusrca, memtoreg,
                  iord, pcen, regwrite, regdst, pcsource, alusrcb, aluop, irwrite);
    input        clk, reset, zero;
    input  [5:0] op;
    output reg       memread, memwrite, alusrca, memtoreg, iord, regwrite, regdst;
    output           pcen;
    output reg [1:0] pcsource, alusrcb, aluop;
    output reg [3:0] irwrite;

    reg [3:0] state, nextstate;
    reg pcwrite, pcwritecond;

    localparam S_FETCH0 = 4'd0,
               S_FETCH1 = 4'd1,
               S_FETCH2 = 4'd2,
               S_FETCH3 = 4'd3,
               S_DECODE = 4'd4,
               S_MEMADR = 4'd5,
               S_MEMRD  = 4'd6,
               S_MEMWB  = 4'd7,
               S_MEMWR  = 4'd8,
               S_R_EX   = 4'd9,
               S_R_WB   = 4'd10,
               S_BEQ    = 4'd11,
               S_JUMP   = 4'd12,
               S_ADDI_EX= 4'd13,
               S_ADDI_WB= 4'd14;

    localparam OP_RTYPE = 6'b000000,
               OP_ADDI  = 6'b001000,
               OP_BEQ   = 6'b000100,
               OP_J     = 6'b000010,
               OP_LB    = 6'b100000,
               OP_SB    = 6'b101000;

    assign pcen = pcwrite | (pcwritecond & zero);

    always @(posedge clk or posedge reset) begin
        if (reset) state <= S_FETCH0;
        else       state <= nextstate;
    end

    always @(*) begin
        nextstate = S_FETCH0;
        case (state)
            S_FETCH0: nextstate = S_FETCH1;
            S_FETCH1: nextstate = S_FETCH2;
            S_FETCH2: nextstate = S_FETCH3;
            S_FETCH3: nextstate = S_DECODE;
            S_DECODE: begin
                case (op)
```

```
            S_DECODE: begin
                case (op)
                    OP_LB, OP_SB: nextstate = S_MEMADR;
                    OP_RTYPE:     nextstate = S_R_EX;
                    OP_BEQ:       nextstate = S_BEQ;
                    OP_J:         nextstate = S_JUMP;
                    OP_ADDI:      nextstate = S_ADDI_EX;
                    default:      nextstate = S_FETCH0;
                endcase
            end
            S_MEMADR:  nextstate = (op == OP_LB) ? S_MEMRD : S_MEMWR;
            S_MEMRD:   nextstate = S_MEMWB;
            S_MEMWB:   nextstate = S_FETCH0;
            S_MEMWR:   nextstate = S_FETCH0;
            S_R_EX:    nextstate = S_R_WB;
            S_R_WB:    nextstate = S_FETCH0;
            S_BEQ:     nextstate = S_FETCH0;
            S_JUMP:    nextstate = S_FETCH0;
            S_ADDI_EX: nextstate = S_ADDI_WB;
            S_ADDI_WB: nextstate = S_FETCH0;
            default:   nextstate = S_FETCH0;
        endcase
    end

    always @(*) begin
        memread = 1'b0; memwrite = 1'b0; alusrca = 1'b0; memtoreg = 1'b0;
        iord = 1'b0; regwrite = 1'b0; regdst = 1'b0; pcsource = 2'b00;
        alusrcb = 2'b00; aluop = 2'b00; irwrite = 4'b0000;
        pcwrite = 1'b0; pcwritecond = 1'b0;

        case (state)
            // Big-endian instruction fetch: byte0 -> instr[31:24], byte3 -> instr[7:0]
            S_FETCH0: begin memread=1'b1; alusrca=1'b0; alusrcb=2'b01; aluop=2'b00; pcwrite=1'b1; pcsource=2'b00; irwrite=4'b1000; end
            S_FETCH1: begin memread=1'b1; alusrca=1'b0; alusrcb=2'b01; aluop=2'b00; pcwrite=1'b1; pcsource=2'b00; irwrite=4'b0100; end
            S_FETCH2: begin memread=1'b1; alusrca=1'b0; alusrcb=2'b01; aluop=2'b00; pcwrite=1'b1; pcsource=2'b00; irwrite=4'b0010; end
            S_FETCH3: begin memread=1'b1; alusrca=1'b0; alusrcb=2'b01; aluop=2'b00; pcwrite=1'b1; pcsource=2'b00; irwrite=4'b0001; end
            S_DECODE: begin alusrca=1'b0; alusrcb=2'b11; aluop=2'b00; end // compute branch/jump target PC + imm<<2
            S_MEMADR: begin alusrca=1'b1; alusrcb=2'b10; aluop=2'b00; end // base + 8-bit imm
            S_MEMRD:  begin memread=1'b1; iord=1'b1; end
            S_MEMWB:  begin regdst=1'b0; memtoreg=1'b1; regwrite=1'b1; end
            S_MEMWR:  begin memwrite=1'b1; iord=1'b1; end
            S_R_EX:   begin alusrca=1'b1; alusrcb=2'b00; aluop=2'b10; end
            S_R_WB:   begin regdst=1'b1; memtoreg=1'b0; regwrite=1'b1; end
            S_BEQ:    begin alusrca=1'b1; alusrcb=2'b00; aluop=2'b01; pcwritecond=1'b1; pcsource=2'b01; end
            S_JUMP:   begin pcwrite=1'b1; pcsource=2'b10; end
            S_ADDI_EX:begin alusrca=1'b1; alusrcb=2'b10; aluop=2'b00; end
            S_ADDI_WB:begin regdst=1'b0; memtoreg=1'b0; regwrite=1'b1; end
        endcase
    end
```

B.4 datapath.v

```
`timescale 1ns/10ps
module datapath(clk, reset, memdata, alusrca, memtoreg, iord, pcen, regwrite,
                regdst, pcsource, alusrcb, irwrite, alucont, zero, instr, adr, writedata);
    input clk, reset;
    input [7:0] memdata;
    input alusrca, memtoreg, iord, pcen, regwrite, regdst;
    input [1:0] pcsource, alusrcb;
    input [3:0] irwrite;
    input [2:0] alucont;
    output zero;
    output [31:0] instr;
    output [7:0] adr, writedata;

    parameter CONST_ZERO = 8'b0;
    parameter CONST_ONE  = 8'b1;

    wire [2:0] ra1, ra2, wa;
    wire [7:0] pc, nextpc, md, rd1, rd2, wd, a, src1, src2, aluresult, aluout, constx4;

    assign ra1 = instr[23:21];      // lower 3 bits of rs field
    assign ra2 = instr[18:16];      // lower 3 bits of rt field
    assign constx4 = {instr[5:0], 2'b00};

    mux23  regmux(instr[18:16], instr[13:11], regdst, wa);
    flopen ir0(clk, irwrite[0], memdata[7:0], instr[7:0]);
    flopen ir1(clk, irwrite[1], memdata[7:0], instr[15:8]);
    flopen ir2(clk, irwrite[2], memdata[7:0], instr[23:16]);
    flopen ir3(clk, irwrite[3], memdata[7:0], instr[31:24]);
    flopenr pcreg(clk, reset, pcen, nextpc, pc);
    flop   mdr(clk, memdata, md);
    flop   areg(clk, rd1, a);
    flop   wrd(clk, rd2, writedata);
    flop   res(clk, aluresult, aluout);

    mux2 adrmux(pc, aluout, iord, adr);
    mux2 src1mux(pc, a, alusrca, src1);
    mux4 src2mux(writedata, CONST_ONE, instr[7:0], constx4, alusrcb, src2);
    mux4 pcmux(aluresult, aluout, constx4, CONST_ZERO, pcsource, nextpc);
    mux2 wdmux(aluout, md, memtoreg, wd);

    regfile rf(clk, regwrite, ra1, ra2, wa, wd, rd1, rd2);
    alu alunlt(src1, src2, alucont, aluresult);
    zerodetect zd(aluresult, zero);
endmodule
```

B.5 flop.v

```
`timescale 1ns/10ps
module flop(clk, d, q);
    input clk;
    input [7:0] d;
    output reg [7:0] q;
    always @(posedge clk) q <= d;
endmodule
```

B.6 flopen.v

```
`timescale 1ns/10ps
module flopen(clk, en, d, q);
    input clk, en;
    input [7:0] d;
    output reg [7:0] q;
    always @(posedge clk) begin
        if (en) q <= d;
    end
endmodule
```

B.7 flopenr.v

```
`timescale 1ns/10ps
module flopenr(clk, reset, en, d, q);
    input clk, reset, en;
    input [7:0] d;
    output reg [7:0] q;
    always @(posedge clk or posedge reset) begin
        if (reset) q <= 8'h00;
        else if (en) q <= d;
    end
endmodule
```

B.8 mips.v

```
`timescale 1ns/10ps
module mips(clk, reset, memdata, memread, memwrite, adr, writedata);
    input clk, reset;
    input [7:0] memdata;
    output memread, memwrite;
    output [7:0] adr, writedata;

    wire [31:0] instr;
    wire zero, alusrca, memtoreg, iord, pcen, regwrite, regdst;
    wire [1:0] aluop, pcsource, alusrcb;
    wire [3:0] irwrite;
    wire [2:0] alucont;

    controller cont(clk, reset, instr[31:26], zero, memread, memwrite, alusrca,
                    memtoreg, iord, pcen, regwrite, regdst, pcsource, alusrcb,
                    aluop, irwrite);
    alucontrol ac(aluop, instr[5:0], alucont);
    datapath dp(clk, reset, memdata, alusrca, memtoreg, iord, pcen, regwrite,
                regdst, pcsource, alusrcb, irwrite, alucont, zero, instr, adr, writedata);
endmodule
```

B.9 mux2.v

```
`timescale 1ns/10ps
module mux2(d0, d1, s, y);
    input s;
    input [7:0] d0, d1;
    output [7:0] y;
    assign y = s ? d1 : d0;
endmodule
```

B.10 mux4.v

```
`timescale 1ns/10ps
module mux4(d0, d1, d2, d3, s, y);
    input [1:0] s;
    input [7:0] d0, d1, d2, d3;
    output reg [7:0] y;
    always @(*) begin
        case (s)
            2'b00: y = d0;
            2'b01: y = d1;
            2'b10: y = d2;
            2'b11: y = d3;
            default: y = d0;
        endcase
    end
endmodule
```

B.11 mux23.v

```
`timescale 1ns/10ps
module mux23(d0, d1, s, y);
    input s;
    input [2:0] d0, d1;
    output [2:0] y;
    assign y = s ? d1 : d0;
endmodule
```

B.12 ram.v

```
`timescale 1ns/10ps
module ram (memdata, memwrite, adr, writedata, clk);
    output reg [7:0] memdata;
    input memwrite;
    input [7:0] adr;
    input [7:0] writedata;
    input clk;

    reg [7:0] mips_ram [0:255];
    integer i;

    initial begin
        for (i = 0; i < 256; i = i + 1) mips_ram[i] = 8'h00;
        $readmemb("/home/ead/G43129353/ece6250/lab8/simulation/testbench/ram.dat", mips_ram);
        memdata = 8'h00;
    end

    always @(negedge clk) begin
        if (memwrite) begin
            mips_ram[adr] = writedata;
            $writememb("ram.after.dat", mips_ram);
        end
        memdata <= mips_ram[adr];
    end
endmodule
```

B.13 regfile.v

```
`timescale 1ns/10ps
module regfile (clk, regwrite, ra1, ra2, wa, wd, rd1, rd2);
    input clk, regwrite;
    input [2:0] ra1, ra2, wa;
    input [7:0] wd;
    output [7:0] rd1, rd2;

    reg [7:0] REGS [0:7];
    integer i;

    initial begin
        for (i = 0; i < 8; i = i + 1) REGS[i] = 8'h00;
    end

    always @(posedge clk) begin
        if (regwrite && (wa != 3'd0)) REGS[wa] <= wd;
    end

    assign rd1 = (ra1 == 3'd0) ? 8'h00 : REGS[ra1];
    assign rd2 = (ra2 == 3'd0) ? 8'h00 : REGS[ra2];
endmodule

```

B.14 zerodetect.v

```
`timescale 1ns/10ps
module zerodetect(a, y);
    input [7:0] a;
    output y;
    assign y = (a == 8'h00);
endmodule
```

B.15 ram.dat

```
00100000
00000001
00000000
00000101
00100000
00000010
00000000
00000011
00000000
00100010
00011000
00100000
00000000
01100010
00100000
00100010
00000000
00100010
00101000
00100100
00000000
00100010
00110000
00100101
00000000
01000001
00111000
00101010
10100000
00000011
00000000
01100100
10000000
00000100
00000000
01100100
00010000
10000011
00000000
00000010
00100000
00000101
00000000
01100011
00001000
00000000
00000000
00001110
00100000
00000110
00000000
01100011
```

```
10100000
00000111
00000000
01100101
00001000
00000000
00000000
00001110
00000000
00000000
00000000
00000000
00001000
00000001
```

```
00000000
00000000
00000000
00000000
```

Appendix C - Testbench

```
`timescale 1ns/10ps

module tb_mips_final;

  reg clk;
  reg reset;

  wire memread;
  wire memwrite;
  wire [7:0] adr;
  wire [7:0] writedata;
  wire [7:0] memdata;

  integer errors;
  integer cycles;

  reg saw_addi;
  reg saw_add;
  reg saw_sub;
  reg saw_and;
  reg saw_or;
  reg saw_slt;
  reg saw_lb;
  reg saw_sb;
  reg saw_beq;
  reg saw_jump;

  mips dut (
    .clk(clk),
    .reset(reset),
    .memdata(memdata),
    .memread(memread),
    .memwrite(memwrite),
    .adr(adr),
    .writedata(writedata)
  );

  ram mem (
    .memdata(memdata),
    .memwrite(memwrite),
    .adr(adr),
    .writedata(writedata),
    .clk(clk)
  );

  always #5 clk = ~clk;

  task check8;
    input [160*8:1] name;
    input [7:0] got;
    input [7:0] exp;
    begin
```

```
    begin
      if (got !== exp) begin
        $display("FAIL: %0s expected=%0d got=%0d at time=%0t", name, exp, got, $time);
        errors = errors + 1;
      end else begin
        $display("PASS: %0s = %0d", name, got);
      end
    end
  endtask

  task check_flag;
    input [160*8:1] name;
    input flag;
    begin
      if (flag !== 1'b1) begin
        $display("FAIL: coverage missing for %0s", name);
        errors = errors + 1;
      end else begin
        $display("PASS: coverage seen for %0s", name);
      end
    end
  endtask

  initial begin
    $shm_open("waves.shm");
    $shm_probe("ACTM");
    $dumpfile("tb_mips_final.vcd");

    $dumpvars(0, tb_mips_final);

    // Important waveform signals for report proof
    $dumpvars(0, dut.cont);
    $dumpvars(0, dut.dp);
    $dumpvars(0, dut.dp.rf);

    clk = 1'b0;
    reset = 1'b1;
    errors = 0;
    cycles = 0;

    saw_addi = 0;
    saw_add  = 0;
    saw_sub  = 0;
    saw_and  = 0;
    saw_or   = 0;
    saw_slt  = 0;
    saw_lb   = 0;
    saw_sb   = 0;
```

```
    saw_sb   = 0;
    saw_beq  = 0;
    saw_jump = 0;

    repeat (3) @(posedge clk);
    reset = 1'b0;

    repeat (220) @(posedge clk);

    $display("\n========== FINAL REGISTER CHECKS ==========");
     //NOTE: dut.dp.rf.REGS is not accessible in gate-level (post-synthesis) simulation
     //because the synthesis tool flattens the REGS array into individual DFF cells.
    // Register checks are skipped for synthesis simulation; use RTL sim to verify registers.
     check8("$s1 addi result", dut.dp.rf.REGS[1], 8'd5);
     check8("$s2 addi result", dut.dp.rf.REGS[2], 8'd3);
     check8("$s3 add result",  dut.dp.rf.REGS[3], 8'd8);
     check8("$s4 lb result",   dut.dp.rf.REGS[4], 8'd8);
     check8("$s5 branch/jump program value", dut.dp.rf.REGS[5], 8'd1);
     check8("$s6 jump program value",        dut.dp.rf.REGS[6], 8'd99);
     check8("$s7 slt result",  dut.dp.rf.REGS[7], 8'd1);

    $display("\n========== FINAL MEMORY CHECKS ==========");
    check8("mem[100] store result", mem.mips_ram[100], 8'd8);
    check8("mem[101] final store result", mem.mips_ram[101], 8'd1);

    $display("\n========== INSTRUCTION COVERAGE CHECKS ==========");
    check_flag("ADDI", saw_addi);
    check_flag("ADD",  saw_add);
    check_flag("SUB",  saw_sub);
    check_flag("AND",  saw_and);
    check_flag("OR",   saw_or);
    check_flag("SLT",  saw_slt);
    check_flag("LB",   saw_lb);
    check_flag("SB",   saw_sb);
    check_flag("BEQ",  saw_beq);
    check_flag("JUMP", saw_jump);

    if (errors == 0) begin
      $display("\n===================================");
      $display("TB_MIPS_FINAL PASSED");
      $display("All arithmetic, logic, load/store, branch, jump, and coverage checks passed.");
      $display("===================================\n");
    end else begin
      $display("\n===================================");
      $display("TB_MIPS_FINAL FAILED errors=%0d", errors);
      $display("===================================\n");
    end
```

```
    $finish;
  end

  always @(posedge clk) begin
    cycles = cycles + 1;

    if (!reset) begin
      // Detect instruction classes from completed instruction register
      case (dut.dp.instr[31:26])
        6'b001000: saw_addi = 1'b1; // addi
        6'b100000: saw_lb   = 1'b1; // lb
        6'b101000: saw_sb   = 1'b1; // sb
        6'b000100: saw_beq  = 1'b1; // beq
        6'b000010: saw_jump = 1'b1; // j

        6'b000000: begin
          case (dut.dp.instr[5:0])
            6'b100000: saw_add = 1'b1;
            6'b100010: saw_sub = 1'b1;
            6'b100100: saw_and = 1'b1;
            6'b100101: saw_or  = 1'b1;
            6'b101010: saw_slt = 1'b1;
          endcase
        end
      endcase
    end

    if (cycles > 300) begin
      $display("FAIL: simulation timeout");
      $finish;
    end
  end

endmodule
```